

1. (§16.2) The current in an RLC circuit is described by


$$\frac{d^2i}{dt^2} + 10 \frac{di}{dt} + 25i = 0$$

If  $i(0) = 2$  and  $di(0)/dt = 0$ , find  $i(t)$  for  $t > 0$ .


2. (§15.6) Use the Laplace transform to solve the following integrodifferential equation.

$$\frac{dy}{dt} + 4y + 3 \int_0^t y \, dt = 6e^{-2t}, \quad y(0) = -1$$

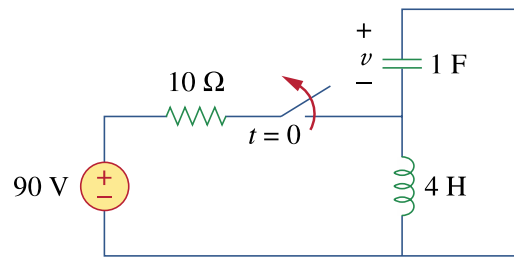
3. (§16.3) Obtain  $v(t)$  for  $t > 0$  for the circuit below. The switch is closed for a long time before  $t = 0$ , then opens at time  $t = 0$ . The 90 V source is DC.



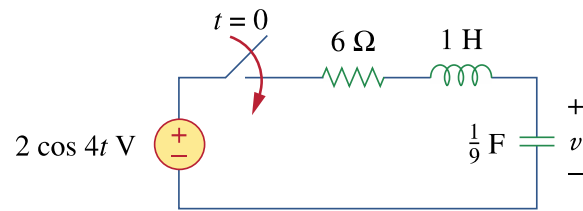4. (§16.3) For the RLC circuit shown below, find the complete response  $v(t)$  if  $v(0) = 2$  V when the switch is closed at  $t = 0$ .



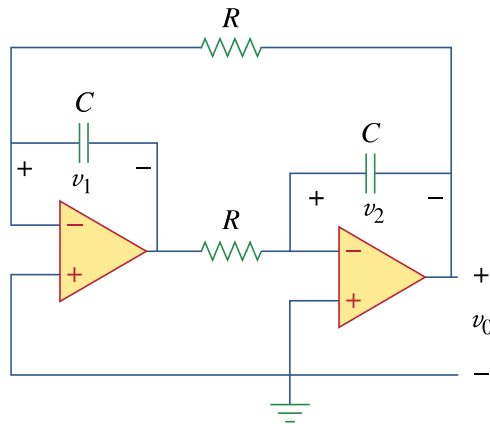5. (§16.3) Given the op amp circuit below, if  $v_1(0^+) = 2 \text{ V}$  and  $v_2(0^+) = 0 \text{ V}$ , find  $v_o$  for  $t > 0$ . Let  $R = 100 \text{ k}\Omega$  and  $C = 1 \mu\text{F}$ .



6. (§16.4) When the input to a system is a unit step function, the response is  $10 \cos 2tu(t)$ . Obtain the transfer function of the system.

7. (§16.4) Obtain the transfer function  $H(s) = V_o/V_s$  for the circuit below.

